

Circuits, Ohm's Law, and Kirchoff's Laws

Lecture 7

1


Circuits

- A circuit is composed of elements (sources, resistors, capacitors, inductors) and conductors (wires).
- Elements are lumped.
- Conductors are perfect.

Lecture 7

2

Schematic

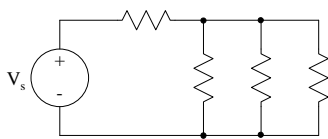

Lecture 7

3

Schematic

- A schematic diagram is an **electrical** representation of a circuit.
- The location of a circuit element in a schematic may have no relationship to its physical location.
- We can rearrange the schematic and have the same circuit as long as the connections between elements remain the same.

Lecture 7

4


Nodes

To find a node, start at a point in the circuit. From this point, everywhere you can travel by moving along perfect conductors is part of a single node.

Lecture 7

5

Example: Find the Nodes

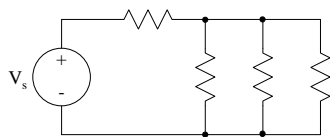

Lecture 7

6

More Nodes

- Since the node is composed of perfect conductors, the voltage (with respect to an appropriate reference) anywhere in a node is the same.

Lecture 7

7

Ohm's Law

Lecture 7

8


Resistors

- A resistor is a circuit element that dissipates electrical energy (usually as heat).
- Real-world devices that are modeled by resistors: incandescent light bulb, heating elements (stoves, heaters, etc.), long wires
- Parasitic resistances: many resistors on circuit diagrams model unwanted resistances in transistors, motors, etc.

Lecture 7

9

The Mathematical Model

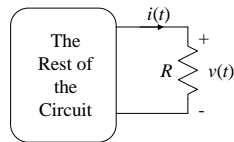

- Resistance measured in Ohms (Ω)
- $v(t) = i(t) R$ - or - $V=IR$
- $p(t) = i^2(t) R = v^2(t)/R$

Lecture 7

10

Example: the 25W Bulb

- If the voltage across a 25W bulb is 120V, what is its resistance?
- What is the current flowing through the 25W bulb?

Lecture 7

11

Thought Question

- When I measured the resistance of a 25W bulb, I got a value of about 40Ω . What's wrong here?

Lecture 7

12

Thought Answer


- The resistance of a wire increases as the temperature increases. For tungsten, the temperature coefficient of resistivity is $4.5 \times 10^{-3}/^{\circ}\text{K}$. A light bulb operates at about 5000°F .

Lecture 7

13

Open Circuit

- What if $R=\infty$?

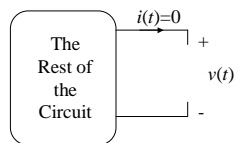


Lecture 7

14

Short Circuit

- What if $R=0$?

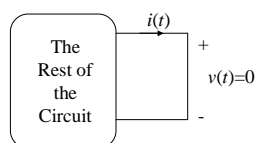

Lecture 7

15

Kirchoff's Laws

Lecture 7

16

Summary

Kirchoff's Current Law (**KCL**) and Kirchoff's Voltage Law (**KVL**) are fundamental properties of circuits that make analysis possible.

Lecture 7

17

Summary

- KCL
 - sum of all currents entering a node is zero
 - sum of currents entering node is equal to sum of currents leaving node
- KVL
 - sum of voltages around any loop in a circuit is zero

Lecture 7

18

KCL Analogy


- Think of a node as being similar to an intersection on a roadway.
- The number of cars entering the intersection must be equal to the number of cars leaving the intersection or else cars will accumulate in the intersection.



Lecture 7

19

KCL Mathematically

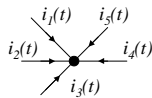


The sum of currents entering the node is zero:

$$\sum_{j=1}^n i_j(t) = 0$$

Lecture 7

20

KCL-Christmas Lights

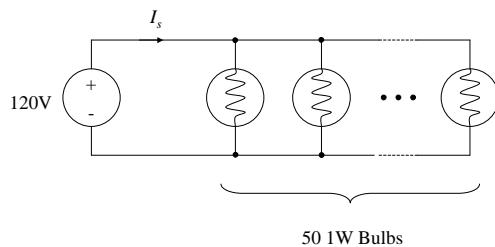

Lecture 7

21

To Solve for I_S :

- Find currents through each light bulb:

$$I_B = 1\text{W}/120\text{V} = 8.3\text{mA}$$

- Apply KCL to the top node:

$$I_S - 50I_B = 0$$

- Solve for I_S :

$$I_S = 50 I_B = 417\text{mA}$$

Lecture 7

22


KVL Analogy

Applying KVL is analogous to taking a walk while paying attention to increases and decreases in altitude. If you walk in a loop (ie. you end your walk where you started) the net change in altitude is zero. This is true for any path that you take for your walk.

Lecture 7

23

KVL

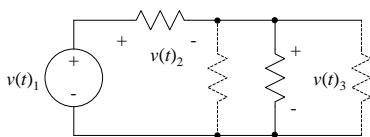

- The sum of voltages around a loop is zero:

$$\sum_{j=1}^n v_j(t) = 0$$

Lecture 7

24


Important Stuff

- A loop is any closed path through a circuit in which no node is encountered more than once.
- A voltage encountered + to - is positive.
- A voltage encountered - to + is negative.

Lecture 7

25

Example-KVL around loop

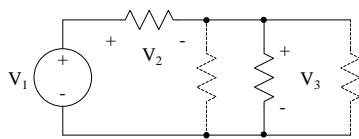


$$-V_1 + V_2 + V_3 = 0$$

Lecture 7

26

A Different Loop

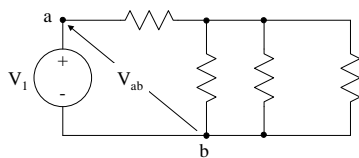

$$\begin{aligned} -V_1 + V_{ab} &= 0 \\ V_1 &= V_{ab} \end{aligned}$$

Lecture 7

27

More Stuff

- Loops need not include circuit elements.
- Arrows represent voltage differences; they point from low to high voltage.

Lecture 7


28

What would happen if you forgot
(or deliberately ignored) the
convention that + to - is positive
and went around a loop using - to
+ is positive?

Lecture 7

29

KVL-Christmas Lights

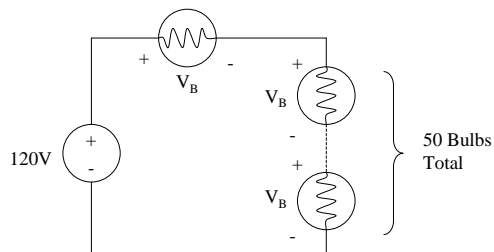

Lecture 7

30


To Solve for V_B

- Apply KVL around the loop:
 $50V_B - 120V = 0$
- Solve for V_B :
 $V_B = 120V/50 = 2.4V$

Lecture 7

31

Example: Thermal Noise

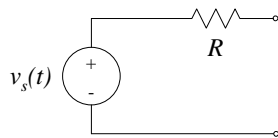


R is a resistor in which charged particles vibrate due to random thermal motion.

Lecture 7

32

Equivalent Model

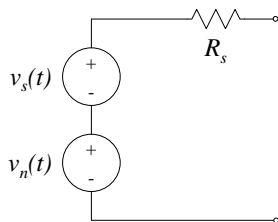

Lecture 7

33


More on the Model

- R_s is an ideal resistor (one in which there is no noise).
- $v_n(t)$ represents the thermal noise in the real resistor.

Lecture 7

34

Equivalent Voltage

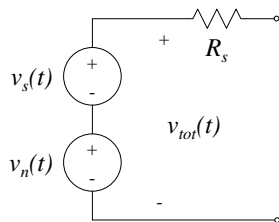

Lecture 7

35

Solve for $v_{tot}(t)$ using KVL

Lecture 7

36
