

Single Loop Circuits and Voltage Division

Lecture 8

1


Single Loop Circuit

- A single loop circuit is one which has only a single loop.
- The same current flows through each element of the circuit-the elements are in series.
- We will consider circuits consisting of voltage sources and resistors.

Lecture 8

2

Example: Christmas Lights

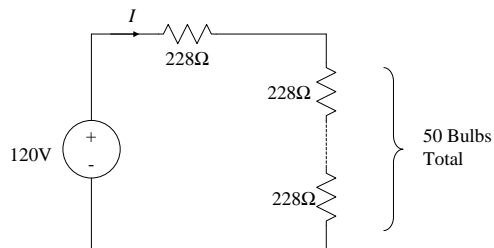

Lecture 8


3

Solve for I

- The same current I flows through the source and each light bulb-how do you know this?
- In terms of I , what is the voltage across each resistor? Make sure you get the polarity right!
- To solve for I , apply KVL around the loop.

Lecture 8

4

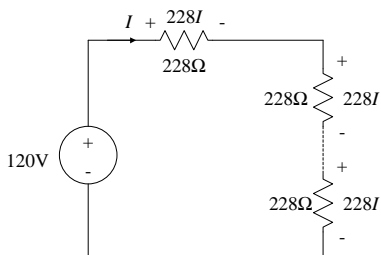

$$228I + 228I + \dots + 228I - 120V = 0$$

$$I = 120V / (50 \times 228\Omega) = 10.5\text{mA}$$

Lecture 8

5


Some Comments

- We can solve for the voltage across each light bulb:
 $V = IR = 10.5\text{mA} \times 228\Omega = 2.4V$
- This circuit has one source and several resistors. The current is:
 Source voltage/sum of resistances
 (Series resistances sum)

Lecture 8

6

Example: Instrumentation

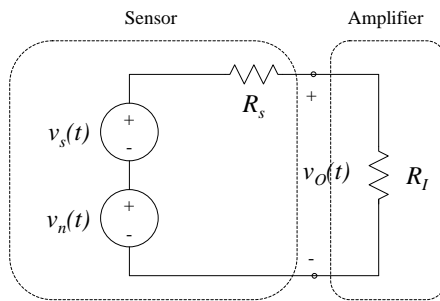

Lecture 8

7


How to Find $v_o(t)$

- Assign a current $i(t)$.
- Assign voltages across the two resistors.
- Use Ohm's law to express the voltages in terms of the current.
- Use KVL around the loop to get an equation for $i(t)$.
- Use Ohm's law to compute $v_o(t)$.

Lecture 8

8

How to Find $v_o(t)$

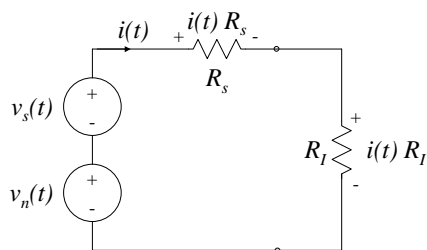

Lecture 8

9

How to Find $v_O(t)$

- Apply KVL around the loop:

$$i(t) R_S + i(t) R_I - v_s(t) - v_n(t) = 0$$

- Solve for $i(t)$:

$$i(t) = \frac{v_s(t) + v_n(t)}{R_S + R_I}$$

Lecture 8

10

How to Find $v_O(t)$

- Use Ohm's law:

$$v_O(t) = R_I i(t) = [v_s(t) + v_n(t)] \frac{R_I}{R_S + R_I}$$

Lecture 8

11

Some Comments

- The current $i(t)$ is:
sum of voltage sources/sum of resistors
- This approach works for any single loop circuit with voltage sources and resistors.

Lecture 8

12

Amplifier Input Resistance


- If R_I is small relative to R_S , what happens to $v_O(t)$?
- If R_I is large relative to R_S , what happens to $v_O(t)$?
- Which condition is preferable, and why?

Lecture 8

13

Voltage Division


Consider two resistors **in series** with a voltage $v(t)$ across them:

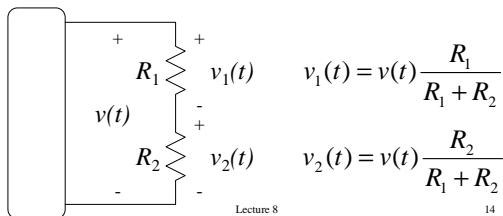

Lecture 8

14

Example: Audio Amplifier

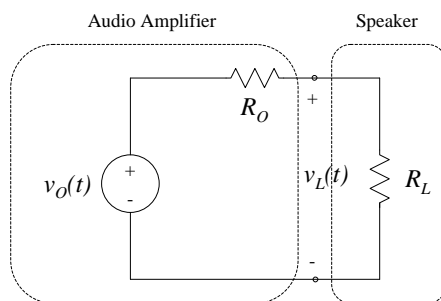

Lecture 8

15

Example: Audio Amplifier

- Find $v_L(t)$ for the following values:

$$v_O(t) = 5V$$

$$R_O = 6\Omega$$

$$R_L = 4\Omega$$

Lecture 8

16

Example: Audio Amplifier

$$v_L(t) = v_O(t) \frac{R_L}{R_O + R_L}$$

$$v_L(t) = 5V \frac{4\Omega}{4\Omega + 6\Omega} = 2V$$

Lecture 8

17

Let $R_O = 4\Omega$ and $v_O(t) = 5V$
Compute the power dissipated in
 R_L for each of the following
values for R_L . Which gives the
highest dissipated power?

$1\Omega, 2\Omega, 3\Omega, 4\Omega,$
 $5\Omega, 6\Omega, 7\Omega, 8\Omega$

Lecture 8

18

Suppose you have three resistors (R_1 , R_2 , and R_3) in series with a voltage $v(t)$ across the series combination. What is the voltage $v_1(t)$ across R_1 ?

Lecture 8

19

Use voltage division to compute the voltage across a Christmas light bulb in a string of 50 identical bulbs. Assume an outlet voltage of 120V.

Lecture 8

20
