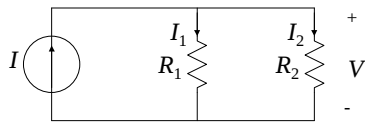


Single Node-Pair Circuits and Current Division

Lecture 9

1

Example: 2 Light Bulbs in Parallel



How do we find I_1 and I_2 ?

Lecture 9

2

Apply KCL at the Top Node

$$I_1 + I_2 = I$$

$$I_1 = \frac{V}{R_1}$$

$$I_2 = \frac{V}{R_2}$$

Lecture 9

3

Solve for V

$$I = \frac{V}{R_1} + \frac{V}{R_2} = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$V = I \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = I \frac{R_1 R_2}{R_1 + R_2}$$

Lecture 9

4

Equivalent Resistance

If we wish to replace the two parallel resistors with a single resistor whose voltage-current relationship is the same, the equivalent resistor has a value of:

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

Lecture 9

5

Now to find I_1

$$I_1 = \frac{V}{R_1} = I \frac{R_2}{R_1 + R_2}$$

- This is the **current divider** formula.
- It tells us how to divide the current through parallel resistors.

Lecture 9


6

What is the formula for I_2 ?

Lecture 9

7

Example: 2 Light Bulbs in Parallel

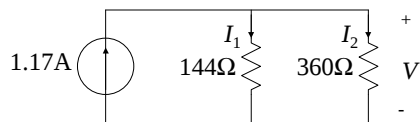

Find I_1 and I_2

Lecture 9

8

I_1 and I_2


$$I_1 = 1.17\text{A} \frac{360\Omega}{144\Omega + 360\Omega} = 0.836\text{A}$$

$$I_2 = 1.17\text{A} \frac{144\Omega}{144\Omega + 360\Omega} = 0.334\text{A}$$

Lecture 9

9

Example: 3 Light Bulbs in Parallel

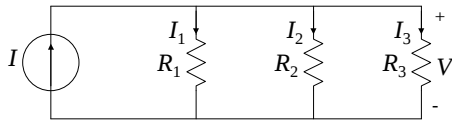

How do we find I_1 , I_2 , and I_3 ?

Lecture 9

10

Apply KCL at the Top Node

$$I_1 + I_2 + I_3 = I$$

$$I_1 = \frac{V}{R_1} \quad I_2 = \frac{V}{R_2}$$

$$I_3 = \frac{V}{R_3}$$

Lecture 9

11

Solve for V

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$V = I \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

Lecture 9

12

$$R_{eq}$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

Lecture 9

13


No Current Divider!

- We cannot make a simple current divider equation for three or more parallel resistors.
- We have to solve for V, then solve for the current(s) of interest.

Lecture 9

14

Example: 3 Light Bulbs in Parallel

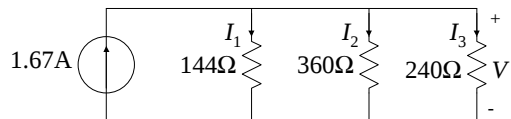

Find I_1

Lecture 9

15

Compute V , then I_1

$$R_{eq} = \frac{1}{\frac{1}{144\Omega} + \frac{1}{360\Omega} + \frac{1}{240\Omega}} = 72\Omega$$


$$V = IR_{eq} = 1.67\text{A} \cdot 72\Omega = 120\text{V}$$

$$I_1 = \frac{V}{R_1} = \frac{120\text{V}}{144\Omega} = 0.833\text{A}$$

Lecture 9

16

More Than One Source

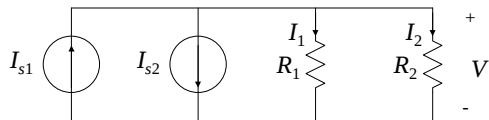

How do we find I_1 or I_2 ?

Lecture 9

17

Apply KCL at the Top Node

$$I_1 + I_2 = I_{s1} - I_{s2}$$

$$I_{s1} - I_{s2} = \frac{V}{R_1} + \frac{V}{R_2} = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$V = (I_{s1} - I_{s2}) \frac{R_1 R_2}{R_1 + R_2}$$

Lecture 9

18

Multiple Current Sources

- We find an equivalent current source by algebraically summing current sources.
- We find an equivalent resistance.
- We find V as equivalent I times equivalent R .
- We then find any necessary currents using Ohm's law.

Lecture 9

19
